

HOMEWORK 6 SOLUTIONS

$$1. (26.16) \quad a) \quad R_{60W} = \frac{V^2}{P} = \frac{(120V)^2}{60W} = 240 \Omega$$

$$R_{200W} = \frac{V^2}{P} = \frac{(120V)^2}{200W} = 72 \Omega$$

$$\Rightarrow I_{60W} = I_{200W} = \frac{\mathcal{E}}{R} = \frac{240V}{(240\Omega + 72\Omega)} = 0.769A$$

$$b) \quad P_{60W} = I^2 R = (0.769A)^2 (240\Omega) = 142W$$

$$P_{200W} = I^2 R = (0.769A)^2 (72\Omega) = 42.6W$$

c) The 60W bulb burns out quickly because the power it delivers (142W) is 2.4 times its rated value.

2. (26.22) From the circuit in Fig. 26.42, we use Kirchhoff's Rules to find the currents, I_1 to the left through the 10V battery, I_2 to the right through the 10Ω resistor:

$$\text{Upper loop: } 10.0V - (2.0\Omega + 3.0\Omega)I_1 - (1.0\Omega + 4.0\Omega)I_2 - 5V = 0$$

$$\Rightarrow I_1 + I_2 = 1.00A$$

$$\text{Lower loop: } 5.0V + (1.0\Omega + 4.0\Omega)I_2 - (10.0\Omega)I_3 = 0$$

$$\Rightarrow I_2 - 2I_3 = -1.0A$$

Along with $I_1 = I_2 + I_3$, we can solve for the three currents and find: $I_1 = 0.8A$, $I_2 = 0.2A$, $I_3 = 0.6A$

$$b) V_{ab} = -(0.2A)(4.0\Omega) - (0.8A)(3.0\Omega) = -3.2V$$

3. (26.25) The total power dissipated in the four resistors of Fig. 26.10a is given by the sum of:

$$P_2 = I^2 R_2 = (0.5A)^2 (2\Omega) = 0.5W,$$

$$P_3 = I^2 R_3 = (0.5A)^2 (3\Omega) = 0.75W$$

$$P_4 = I^2 R_4 = (0.5A)^2 (4\Omega) = 1W$$

$$P_7 = I^2 R_7 = (0.5A)^2 (7\Omega) = 1.8W$$

$$\Rightarrow P_{\text{total}} = P_2 + P_3 + P_4 + P_7 = 4W$$

4. (26.37) a) $i = q/RC = 1.12 \times 10^{-4} A$


b) $\tau = RC = 5.82 \times 10^{-4} s$

5. (26.55) Circuit (a)

The 75Ω and 40Ω resistors are in parallel and have equivalent resistance 26.09Ω

The 25Ω and 50Ω resistors are in parallel and have equivalent resistance 16.67Ω

The network is equivalent to:


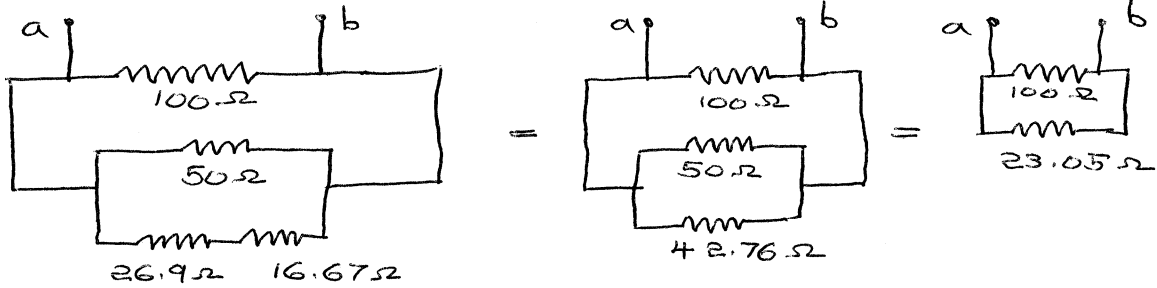


$$\frac{1}{R_{eq}} = \frac{1}{100\Omega} + \frac{1}{23.05\Omega} \quad \text{so} \quad R_{eq} = 18.7\Omega$$

Circuit (b)

The 30.0Ω and 45.0Ω resistors are in parallel and have equivalent resistance 18.0Ω

The network is equivalent to :

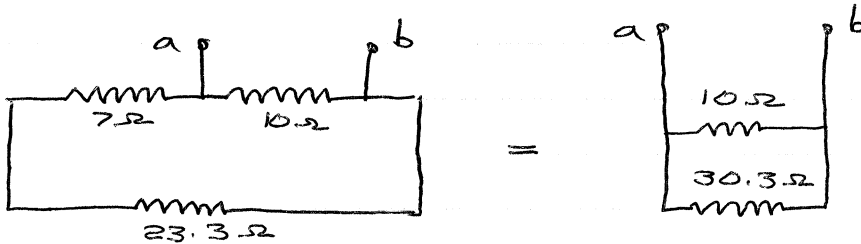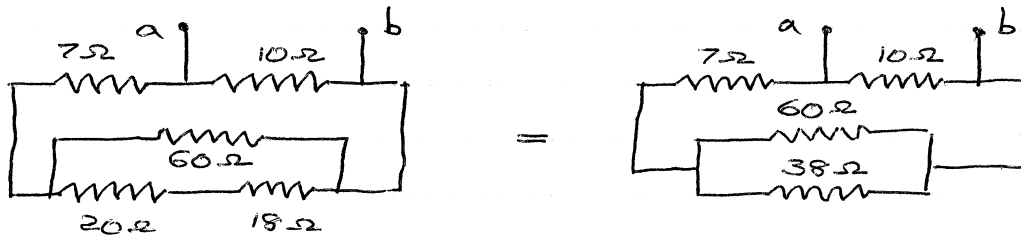

$$\frac{1}{R_{eq}} = \frac{1}{10\Omega} + \frac{1}{30.3\Omega} \quad \text{so} \quad R_{eq} = 7.5\Omega$$