

PHY 212 General Physics II - Electricity, Magnetism and Light  
Summer 2007

Quiz 7 Thursday, Aug 02

Name: WORKED OUT COPY

1. (6 points) Current in an  $L$ - $R$  series circuit with an emf  $\mathcal{E}$  and time constant  $\tau = L/R$  is

$$i = \frac{\mathcal{E}}{R}(1 - e^{-t/\tau}) \quad (1)$$

- (i) Current in the circuit at time  $t = 0$  is:

$$i(t=0) = \frac{\mathcal{E}}{R}(1 - e^0) = \frac{\mathcal{E}}{R}(1 - 1) = 0$$

- (ii) Current in the circuit after one time constant  $\tau$  is:

$$i(t=\tau) = \frac{\mathcal{E}}{R}(1 - e^{-\tau/\tau}) = \frac{\mathcal{E}}{R}(1 - \frac{1}{e})$$

- (iii) Current in the circuit as time  $t \rightarrow \infty$  is:

$$i(t \rightarrow \infty) = \frac{\mathcal{E}}{R}(1 - e^{-\infty}) = \frac{\mathcal{E}}{R}(1 - 0) = \frac{\mathcal{E}}{R}$$

2. (9 points) The instantaneous charge  $q$  in the capacitor of an  $L$ - $C$  circuit is given by

$$q = Q \cos(\omega t + \phi) \quad (2)$$

where  $\omega = \sqrt{1/LC}$ . Show that (i)  $\frac{1}{2}Li^2 + \frac{q^2}{2C} = \frac{Q^2}{2C}$  and (ii)  $\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$ .

$$(i) i = \frac{dq}{dt} = -\omega Q \sin(\omega t + \phi)$$

$$\begin{aligned} \frac{1}{2}Li^2 + \frac{q^2}{2C} &= \frac{1}{2}L\omega^2Q^2 \sin^2(\omega t + \phi) + \frac{Q^2 \cos^2(\omega t + \phi)}{2C} \\ &= \frac{1}{2}L \frac{1}{LC} Q^2 \sin^2(\omega t + \phi) + \frac{Q^2}{2C} \cos^2(\omega t + \phi) \\ &= \frac{Q^2}{2C} [\sin^2(\omega t + \phi) + \cos^2(\omega t + \phi)] \\ &= \frac{Q^2}{2C} \end{aligned}$$

$$(ii) \frac{d^2q}{dt^2} = -\omega^2 Q \cos(\omega t + \phi) = -\frac{1}{LC} q$$

$$\therefore \frac{d^2q}{dt^2} + \frac{1}{LC} q = -\frac{1}{LC} q + \frac{1}{LC} q = 0$$