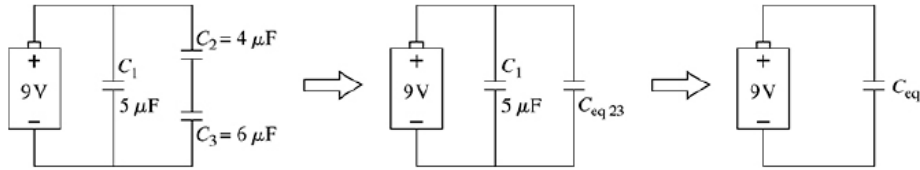


30.62. Model: Assume the battery is an ideal battery.

Visualize:



The pictorial representation shows how to find the equivalent capacitance of the three capacitors shown in the figure.

Solve: Because C_2 and C_3 are in series,

$$\frac{1}{C_{\text{eq}23}} = \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{4 \mu\text{F}} + \frac{1}{6 \mu\text{F}} = \frac{10}{24} (\mu\text{F})^{-1} \Rightarrow C_{\text{eq}23} = \frac{24}{10} \mu\text{F} = 2.4 \mu\text{F}$$

$C_{\text{eq}23}$ and C_1 are in parallel, so

$$C_{\text{eq}} = C_{\text{eq}23} + C_1 = 2.4 \mu\text{F} + 5 \mu\text{F} = 7.4 \mu\text{F}$$

A potential difference of $\Delta V_C = 9 \text{ V}$ across a capacitor of equivalent capacitance $7.4 \mu\text{F}$ produces a charge

$$Q = C_{\text{eq}} \Delta V_C = (7.4 \mu\text{F})(9 \text{ V}) = 66.6 \mu\text{C}$$

Because C_{eq} is a parallel combination of C_1 and $C_{\text{eq}23}$, these capacitors have $\Delta V_1 = \Delta V_{\text{eq}23} = \Delta V_C = 9 \text{ V}$. Thus the charges on these two capacitors are

$$Q_1 = (5 \mu\text{F})(9 \text{ V}) = 45 \mu\text{C} \quad Q_{\text{eq}23} = (2.4 \mu\text{F})(9 \text{ V}) = 21.6 \mu\text{C}$$

Because $Q_{\text{eq}23}$ is due to a series combination of C_2 and C_3 , $Q_2 = Q_3 = 21.6 \mu\text{C}$. This means

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{21.6 \mu\text{C}}{4 \mu\text{F}} = 5.4 \text{ V} \quad \Delta V_3 = \frac{Q_3}{C_3} = \frac{21.6 \mu\text{C}}{6 \mu\text{F}} = 3.6 \text{ V}$$

In summary, $Q_1 = 45 \mu\text{C}$, $V_1 = 9 \text{ V}$; $Q_2 = 21.6 \mu\text{C}$, $V_2 = 5.4 \text{ V}$; and $Q_3 = 21.6 \mu\text{C}$, $V_3 = 3.6 \text{ V}$.

30.68. Model: Assume the battery is an ideal battery.

Visualize: Please refer to Figure P30.68. The battery is connected to two series capacitors C_1 and C_2 .

Solve: The equivalent capacitance is

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow C_{\text{eq}} = \frac{C_1 C_2}{C_1 + C_2}$$

Because the charge on capacitor C_2 is $450 \mu\text{C}$, the charge on C_{eq} and C_1 is also $450 \mu\text{C}$. We have

$$\Delta V_{\text{eq}} = \frac{Q_{\text{eq}}}{C_{\text{eq}}} \Rightarrow 60 \text{ V} = \frac{450 \mu\text{C}}{C_1 C_2 / (C_1 + C_2)} = \frac{(450 \mu\text{C})(12 \mu\text{F} + C_2)}{(12 \mu\text{F}) C_2} \Rightarrow C_2 = \frac{(450 \mu\text{C})(12 \mu\text{F})}{720 \mu\text{C} - 450 \mu\text{C}} = 20 \mu\text{F}$$

Assess: Note that capacitors connected in series have the same charge.

30.70. Solve: The magnitude of the work done by the external force is equal to the change in the electric potential energy of the capacitor. The work done is

$$W_{\text{force}} = \Delta U = U_2 - U_1 = \frac{1}{2} \frac{Q^2}{C_2} - \frac{1}{2} \frac{Q^2}{C_1}$$

Note that the charge on the plates is not changed as the distance between the electrodes is changed. Thus,

$$W_{\text{force}} = \frac{1}{2} Q^2 \left[\frac{1}{C_2} - \frac{1}{C_1} \right] = \frac{1}{2} (4.0 \times 10^{-3} \text{ C})^2 \left[\frac{1}{2.0 \mu\text{F}} - \frac{1}{5.0 \mu\text{F}} \right] = 2.4 \text{ J}$$

Assess: The work done on the capacitor is stored as electric potential energy in the capacitor.

30.72. Solve: The energy density in the electric field at the surface of the sphere is $u = \frac{1}{2} \epsilon_0 E^2$, where E is the electric field strength at the surface. The electric field strength and the potential on the surface of the sphere are related as follows:

$$E = \frac{1}{4\pi\epsilon_0} \frac{Q}{R^2} = \left(\frac{1}{4\pi\epsilon_0} \frac{Q}{R} \right) \frac{1}{R} = \frac{V}{R} = \frac{1000 \text{ V}}{5.0 \times 10^{-3} \text{ m}} = 2.0 \times 10^5 \text{ N/m}$$

$$\Rightarrow u = \frac{1}{2} (8.85 \times 10^{-12} \text{ C}^2/\text{Nm}^2) (2.0 \times 10^5 \text{ V/m})^2 = 0.177 \text{ J/m}^3$$