

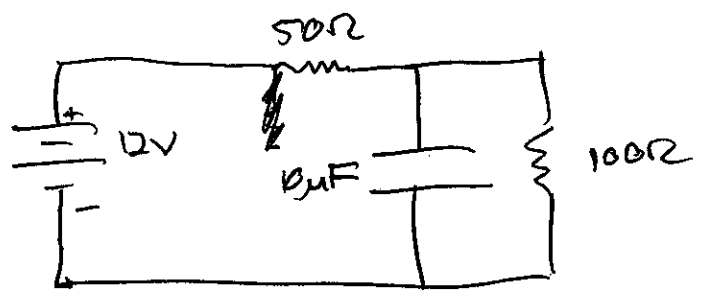


32-1 Circuit diagrams

32-2

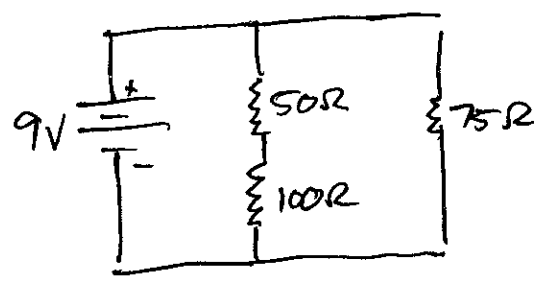

32-3 use $V=IR$

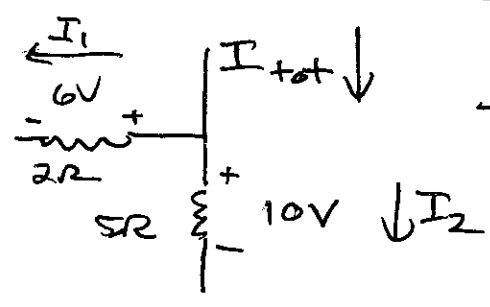


$$I_1 = \frac{6V}{2\Omega} = 3A$$


$$I_2 = \frac{10V}{5\Omega} = 2A$$

$$I_{tot} = I_1 + I_2 = 5A \text{ downwards}$$

32-4

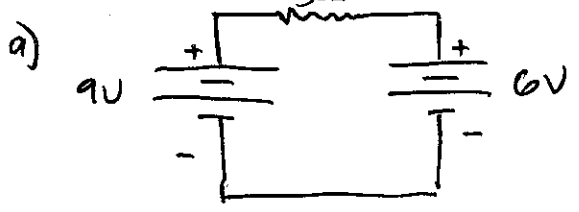

~~Kirchhoff~~ equivalent circuit:


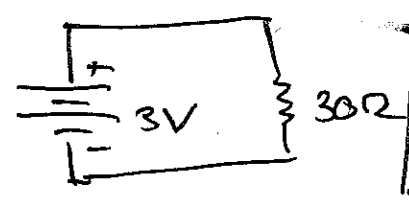


$V=IR$


$$I = \frac{3V}{30\Omega} = 0.1A$$

~~clockwise~~ clockwise


b)

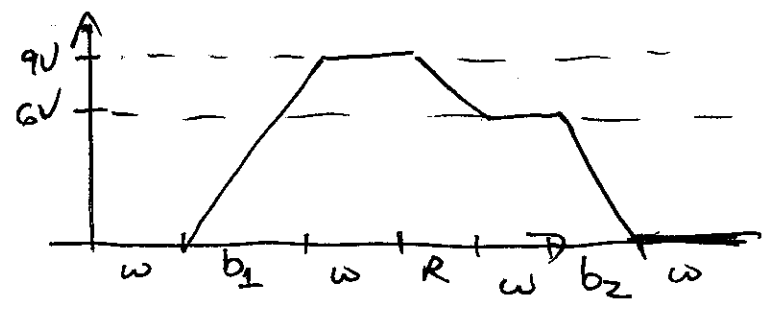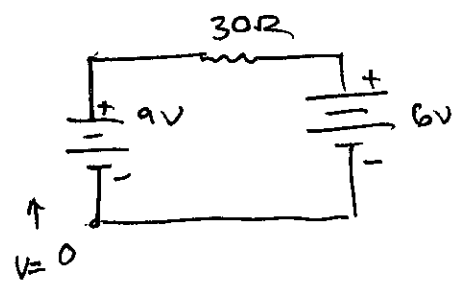

32-6

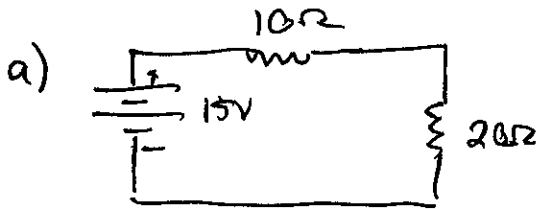


eq. circuit

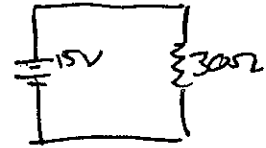


$$V = IR \Rightarrow I = 0.5 \text{ A}$$

$$V_{(10\Omega)} = (0.5 \text{ A})(10\Omega) = 5 \text{ V}$$
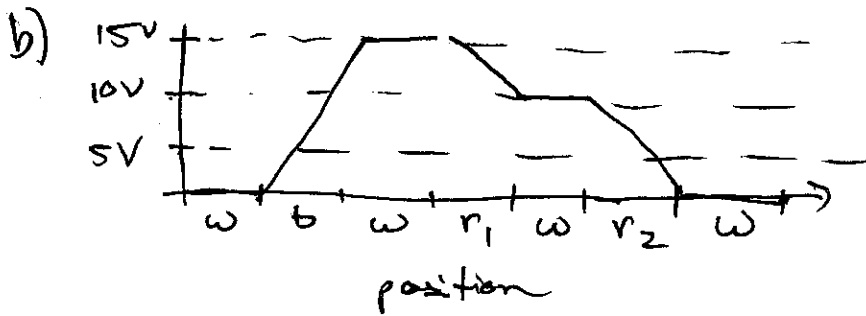
$$V_{(20\Omega)} = (0.5 \text{ A})(20\Omega) = 10 \text{ V}$$



32-8

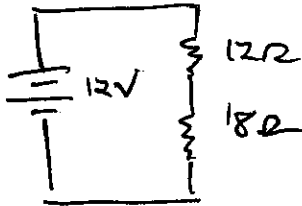


$$R_{\text{tot}} = 30\Omega, \quad I = \frac{12\text{V}}{30\Omega}$$

$$P = I^2 R$$

$$P_1 = I^2 R_1 = \left(\frac{12\text{V}}{30\Omega}\right)^2 12\Omega = 1.92 \text{ W}$$

$$P_2 = I^2 R_2 = \left(\frac{12\text{V}}{30\Omega}\right)^2 18\Omega = 2.88 \text{ W}$$

32-14

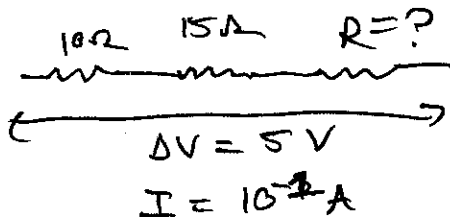


$$R_{\text{tot}} = R + 10\Omega + 15\Omega = R + 25\Omega$$

and $\Delta V = IR_{\text{tot}}$

$$5\text{V} = (10^{-2} \text{ A})(R + 25\Omega)$$

$$\Rightarrow \boxed{R = 25\Omega}$$

32.17

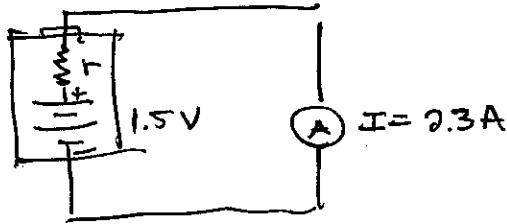

$$V = IR$$

$$r = \frac{1.5V}{2.3A} = .65\Omega$$

$$P = I^2 R$$

$$= (2.3A)^2 (.65\Omega)$$

$$P = 3.4W$$

32-21

resistors in parallel:

$$R_{\text{tot}} = \left[\frac{1}{R} + \frac{1}{R} + \frac{1}{200\Omega} \right]^{-1} = 75\Omega$$



$$\frac{(200\Omega)R}{2(200\Omega) + R} = 75\Omega$$

solve for R:

$$(125\Omega)R = 2(200\Omega)(75\Omega)$$

$$R = 240\Omega$$

32-23

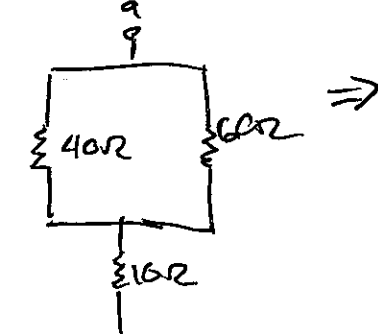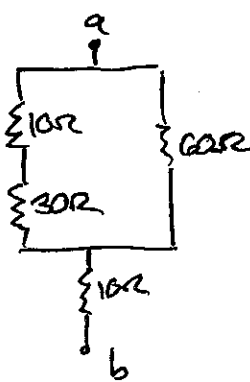

using 10Ω and 30Ω
in series
($R_1 + R_2$)

using 40Ω and
60Ω in parallel
 $\left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$

using 24Ω and 10Ω
in series
 $R_1 + R_2$

$$R_{ab} = 34\Omega$$