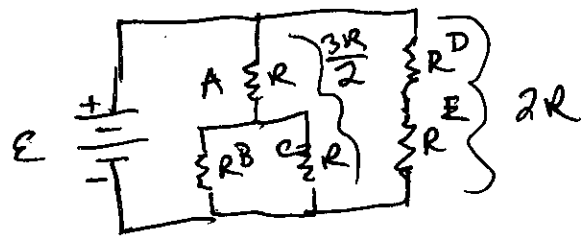


WORKSHOP 10.2

3/20/2009

32-36 Each light bulb is a resistor



$$V_{ABC} = E$$

$$I_A = \frac{E}{\frac{3R}{2}} = \frac{2E}{3R}$$



$$I_B = I_C = \frac{E}{3R}$$

$$I_D = I_E = \frac{E}{2R}$$


so $I_A > I_D = I_E > I_B = I_C$

⇒ order of brightness $A > D = E > B = C$

32-42

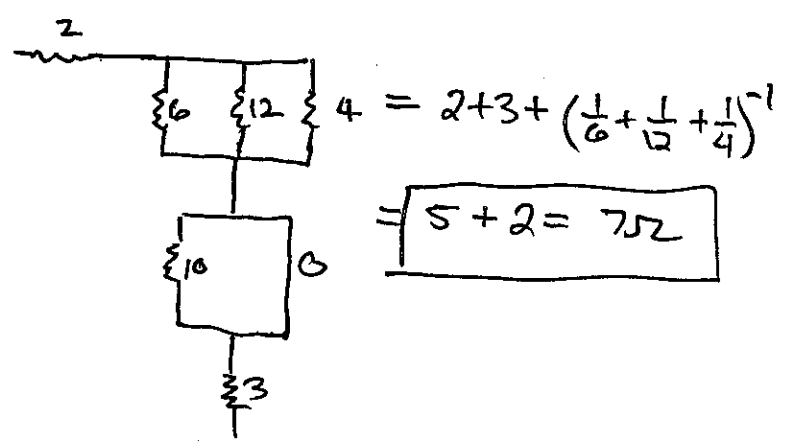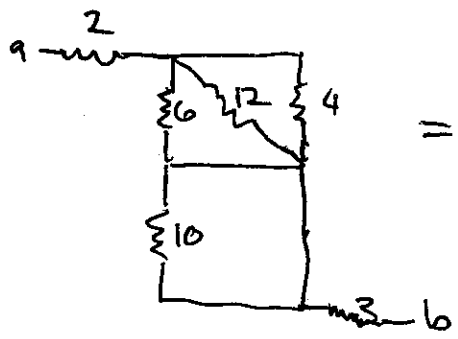

32-48

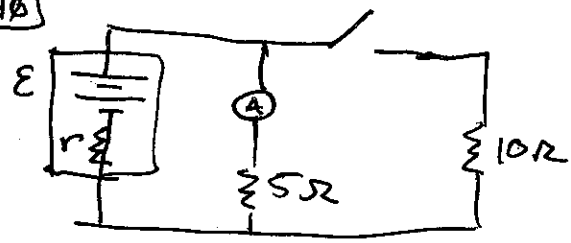

open, $I_0 = 1.636 A$
closed $I_c = 1.565 A$

open $E = I R_{tot} = I_0 (5+r)$

closed want $\Delta V_{5\Omega}$: $R_{tot} = r + (\frac{1}{5} + \frac{1}{10})^{-1} \Omega = r + \frac{10}{3} \Omega$


$$I_{tot} = \frac{E}{r + \frac{10}{3} \Omega} \Rightarrow \Delta V = \frac{E r}{r + \frac{10}{3} \Omega} \quad \Delta V = E \left(1 - \frac{r}{r + \frac{10}{3} \Omega} \right)$$

and $I_c = \frac{\Delta V}{5\Omega} = \frac{E}{5\Omega} \left(\frac{10/3 \Omega}{r + 10/3} \right) = \frac{I_0 (5+r)}{5} \left(\frac{10/3}{r + 10/3} \right)$

$r = 0.5 \Omega$
 $E = 9 V$

32-74

a)

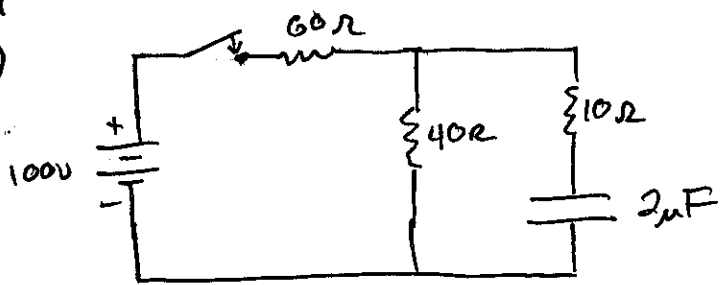

at steady state w/ closed switch, capacitor allows no current in rt. half of circuit ($I_{rt}=0$)

thus $V = I_{left} (60\Omega + 40\Omega) = 100V \Rightarrow I_{left} = 1A$


Voltage drop across 60Ω resistor = $60V$

and capacitor is in ||, thus capacitor has $\Delta V = 40V$

$$Q = C \Delta V_c = (2 \times 10^{-6} F) (40V) = 80 \times 10^{-6} C = 80 \mu C$$

b) Switch opened at $t=0$

now circuit is just

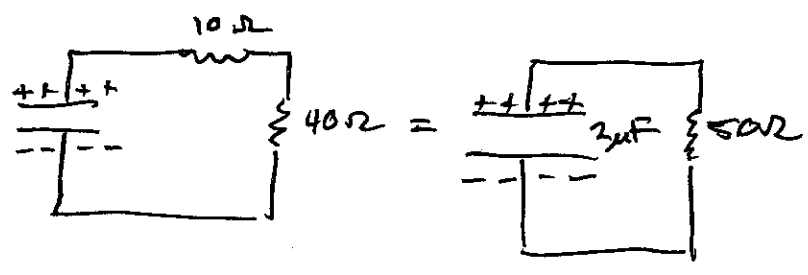

now $Q = Q_0 e^{-t/\tau}$ with $\tau = CR$

$Q = 0.1 \cdot Q_0$

$\Rightarrow .1 = e^{-t/\tau}$

or $\log(.1) = -\frac{t}{\tau}$

$t = \tau \log(10) = (2 \times 10^{-6} F) (50 \Omega) \log(10) = 2.3 \times 10^{-4} s$

$t = .23 ms$